

## UNIT-1: Binary Systems

### Short Questions:

- 1) Convert  $(367.52)_{10}$  to binary and  $(1001011)_2$  to Decimal.
- 2) Convert  $(A6C7)_{16}$  to binary and  $(11000101011010)_2$  to hexadecimal.
- 3) Convert  $(110101.101010)_2$  to octal and  $(367)_8$  to binary.
- 4) Find out 10's and 9's complement of 572.
- 5) Convert  $(378.93)_{10}$  to octal and  $(0.1376)_8$  to Decimal 6) Perform binary addition:  $(11011011)_2 + (01011101)_2$  7)  $(111.1)_2 * (10.1)_2 = ( )_2$
- 8) Divide  $(11011)_2$  by  $(10.1)_2$ .
- 9) Convert  $(97)_{10}$  to excess-3 code.
- 10) Convert  $(1762.46)_8$  to hexadecimal and  $(3.E)_{16}$  to Octal 11.) Convert BINARY to GRAY. (i) 11011

### Long Questions:

- 1) Explain 1's complement and 2's complement with suitable Example. Show the subtraction using complements.
- 2) If (i) 2's complement of a binary number is 0111, obtain the original Number. (ii) 10's complement of decimal number is 625, obtain Original number.
- 3) For 0 to 9 decimal numbers, write down a table of corresponding BCD and excess-3 code.
- 4) Explain Gray code.

**UNIT-2: Binary Logic and Boolean Algebra****Short Questions:**

- 1) Define: Logic Circuit, Logic Gate.
- 2) Draw logic circuit for following expression  $F=AB'+A'C$ . 3) (i)  $A+BC =$ \_\_\_\_\_, (ii)  $(A+B)' =$ \_\_\_\_\_.
- 4) Write any two postulates related to Boolean algebra.
- 5) Simplify:  $A(A'+C)(A'B+C')$ .
- 6) Define: Bubbled gate.
- 7) State the De-Morgan's theorems.

**Long Questions:**

- 1) Explain all logic gates.
- 2) Explain NOR as a universal gate.
- 3) Explain NAND as a universal gate.
- 4) Explain absorption & distributive property of Boolean algebra.
- 5) State and prove De-Morgan's theorems.
- 6) Draw the logic circuit using basic gates  $Y = (A'+B'+C)(A+B'+C)$ .
- 7) Simplify the equation  $Y=AB+ABC+A'$  using Boolean algebra.

**UNIT-3: Boolean Function Implementation****Short questions:**

1. Define Max term, Min term.
2. Define: Don't care Variable.
3. Define SOP, POS.
4. What is K-map?
5. Draw K-map for 3 variables.
6. What is the application of K-map?
7. Define Product term, Sum term.

**Long questions:**

1. With suitable examples explain canonical or standard form.
2. Simplify and draw a digital circuit for the following equation.

$$F = \sum m(0,2,6,10,11,12,13) \text{ Don't care } d(3,4,14,15)$$

3. Simplify POS expression using K-map method for

$$F(A, B, C, D) = \prod m(0, 1, 8, 9, 10) \text{ and implement using NOR logic.}$$

4. Discuss needs of simplification of Boolean equations in digital systems.
5. Simplify following Boolean function in SOP form using K-map and implement using logic gates.

$$F(A, B, C, D) = \sum m(1, 4, 6, 9, 10, 11, 14, 15)$$

6. Minimize the following Boolean function using K-map  $F(A, B, C, D) = \prod m(1, 2, 3, 8, 9, 10, 11, 14).d(7, 15)$

7. Obtain simplified SOP expression using K-map method for

$\sum m(0, 1, 3, 4, 5, 6, 11, 14)$  and implement using NAND logic

8. Represent the following Boolean expression in SOP form. Also prepare a K- map for it.
9. Represent the following expression in POS form.

$$Y = (A+C'+D')(A'+C')(B'+D')$$

### UNIT-4: Basic Combinational Logic

#### Short questions:

1. What is combinational logic?
2. Define: adder circuit and subtractor circuit.
3. Define: half subtractor and full subtractor.
4. Define: half adder and full adder.

#### Long questions:

1. Draw half adder circuit and write its truth table.
2. Draw and explain Binary 4-bit parallel adder circuit.
3. Explain half subtractor with its block diagram and draw a logic circuit of full subtractor using two half subtractor.
4. Explain 4-2 Encoder.
5. Explain 2-4 Decoder.
6. Explain 4-1 Multiplexer.
7. Explain 1-4 Demultiplexer.

**UNIT-5: Basic Sequential circuits****Short questions:**

1. Compare combinational circuit and sequential circuit.
2. State main types of flip flop
3. Draw symbol of clocked RS flip-flop

**Long questions:**

1. Explain SR flip flop with symbol, logic circuit & truth table.
2. Explain JK flip flop with symbol, logic circuit & truth table.
3. Explain D flip flop with symbol, logic circuit & truth table.
4. Explain T flip flop with symbol, logic circuit & truth table.